

Electric Druid Tap Tempo LFO


Introduction	1
Features	2
<i>Simple “Tap Tempo” control</i>	2
<i>Ability to synchronize LFO to external clocks</i>	2
<i>LFO range from 0.025Hz to above 100Hz</i>	2
<i>8 output waveforms</i>	2
<i>Half-speed, Double-speed, and Triplets</i>	2
<i>Wave Distort CV input</i>	3
<i>19.5KHz sample output rate</i>	3
<i>8-bit resolution on the control voltages</i>	3
<i>Logarithmic control response over 1:256 range</i>	3
Pinout Diagram	4
Application Notes	5
<i>Modular synth LFO with tap tempo and sync input</i>	5
<i>Simple tap tempo drum machine or sequencer clock</i>	6
<i>Tap tempo LFO control of vactrols or LED/LDRs</i>	6
<i>Tap tempo tremolo circuit</i>	7
<i>Disabling unwanted CV inputs</i>	8
<i>Using rotary switches to select waveform or multiplier</i>	8
<i>Using the Tap Tempo LFO as a synch-able LFO</i>	8

Introduction

This low frequency oscillator uses a PIC microprocessor to create a versatile tap tempo LFO. All LFO parameters are controlled by 0-5V control voltages.

The chip can produce 8 waveforms including a random (sample-and-hold) waveform. The basic LFO tempo is controlled by TEMPO CV or TAP TEMPO IN. The final output frequency is based on this setting and the MULTIPLIER CV, which allows you to set a basic tempo, and then produce an LFO output at a multiple of this speed.

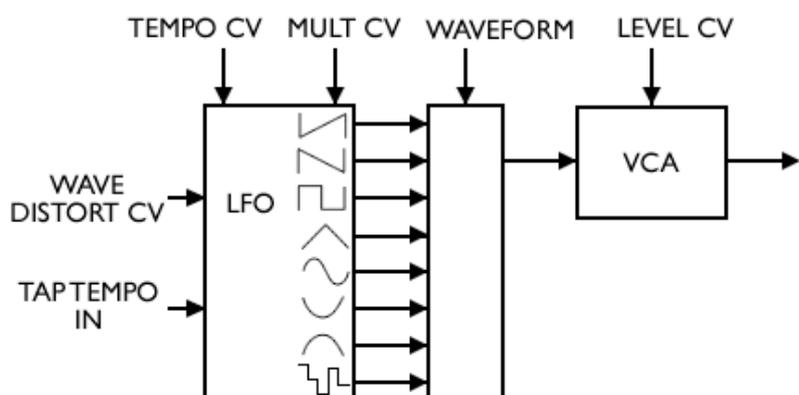The WAVEFORM voltage selects one of the 8 waveforms. The LFO waveforms can be modified by the WAVE DISTORT CV. Finally, the LEVEL CV sets the output level.



Features

Simple “Tap Tempo” control

The TAP TEMPO input can measure the time between two taps of a momentary switch or button, and uses this time to set the LFO’s basic tempo.

Ability to synchronize LFO to external clocks

The TAP TEMPO input can also accept 0-5V pulses. This allows the LFO to be synchronized to an external clock.

LFO range from 0.025Hz to above 50Hz

The basic range of the TEMPO CV allows the LFO to produce frequencies between 0.05Hz (a 20 second cycle) and 12.8Hz. However, in conjunction with the MULTIPLIER CV, this range is extended to 0.025Hz (a 40-second cycle) to 100Hz.

8 output waveforms

The chip can produce 8 output waveforms, shown below. These are selected by the voltage on Pin 12 (WAVEFORM).




Half-speed, Double-speed, and Triplets

The MULTIPLIER CV input selects a tempo multiplier which is used to determine the final LFO frequency. This allows the LFO to produce changes at double or half-speed, or produce triplet times. The available multipliers are shown below:

Multiplier	Musical symbol	Note name
0.5		1/2 note, minim
1		1/4 note, crotchet
1.5		Triplet 1/4 note, triplet crotchet
2		1/8 th note, quaver
3		Triplet 1/8 th note, triplet quaver
4		1/16 th note, semiquaver

Wave Distort CV input

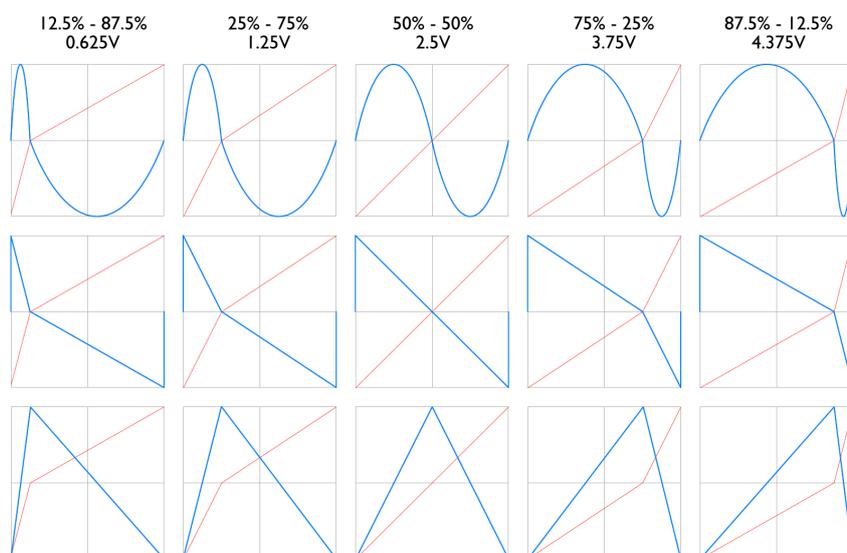The selected waveform can be distorted using the WAVE DISTORT input. This modifies the duty cycle of all LFO waveforms. Examples are shown below.



The top row shows the effect of the WAVE DISTORT CV on the SINE wave, whilst the following rows show the effect on the RAMP DOWN and TRIANGLE waveforms. Other waves (excepting RANDOM) are affected similarly.

10-bit LFO output resolution

The internal waveforms and calculations are 8-bit, but the chip interpolates between the given values to provide a 16-bit output, of which 10 bits are fed to the PWM module.

19.5KHz sample output rate

The PWM frequency is around 19.5KHz. This allows the PWM output to be heavily filtered for a smooth analogue output. The two-stage 24dB Bessel filter provides the best-possible pulse filtering.


8-bit resolution on the control voltages

The Sequential Prophet 5 used a 7-bit control resolution, so this is going slightly better. Whether a standard potentiometer actually has the accuracy to directly produce an 8 bit resolution is another question. The inputs are sampled at over 6KHz.

Logarithmic control response over 1:256 range

The Tempo CV gives the full range from 0.05 Hz to 12.8 Hz in eight even octaves, eg 0.05-0.1Hz, 0.1-0.2Hz, 0.2-0.4Hz, 0.4-0.8Hz, 0.8-1.6Hz, 1.6-3.2Hz, 3.2-6.4Hz, 6.4-12.8Hz.


Pinout Diagram

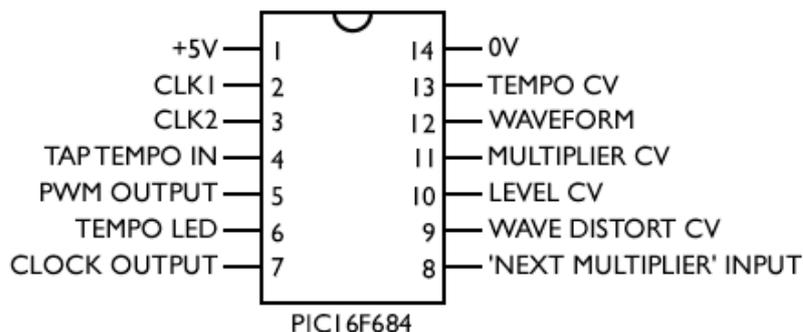

Pin	Function	Details	Notes
1	+5V	Power supply	
2	CLK1	Connect to Xtal	20MHz Clock
3	CLK2	Connect to Xtal	20MHz Clock
4	TAP TEMPO IN	5-0V digital input	Sets basic tempo of LFO. Note that this input expects negative-going pulses.
5	PWM OUTPUT	0-5V digital output	PWM output at 19.5KHz
6	TEMPO LED	0-5V digital output	Indicates tap timing (on when timing)
7	CLOCK OUTPUT	0-5V digital output	Provides a 0-5V signal at the current LFO frequency
8	NEXT MULTIPLIER	0-5V digital input	Steps through Multiplier values 0-5. Expects negative-going pulses.
9	WAVE DISTORT CV	0-5V analogue input	8 bit, values from 0 to 255 Alters waveshape of LFO waveforms. Does not affect RANDOM wave.
10	LEVEL CV	0-5V analogue input	8 bit, values from 0 to 255 Controls overall output level
11	MULTIPLIER CV	0-5V analogue input	3 bit, values from 0-5 Note that values 6 & 7 are not used (set to x1) so the maximum useful CV is 3.75V
12	WAVEFORM	0-5V analogue input	3 bit, values from 0 to 7
13	TEMPO CV	0-5V analogue input	8 bit, values from 0 to 255 0.05 Hz to 12.8 Hz for LFO
14	0V	Power supply	

Simple tap tempo drum machine or sequencer clock

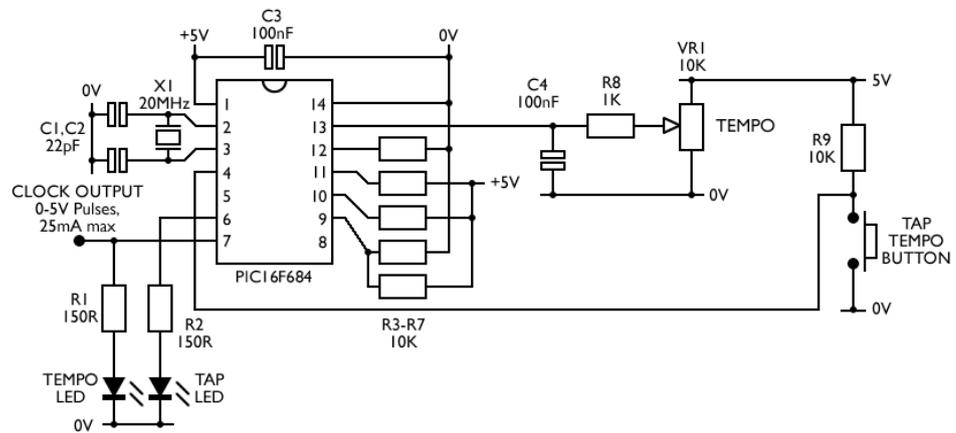
This example circuit provides tap-tempo +5V clock pulses for driving analogue sequencers or drum machines.



R2 to R6 disable the waveform output (fixed to Ramp Up), the multiplier (fixed to x1), the output level (fixed to max), and the pulse width (fixed to 2.5V, square). The main LFO output isn't used. Tempo can be set either by the Tempo knob VR1 or by tapping the button.

Tap tempo LFO control of vactrols or LED/LDRs

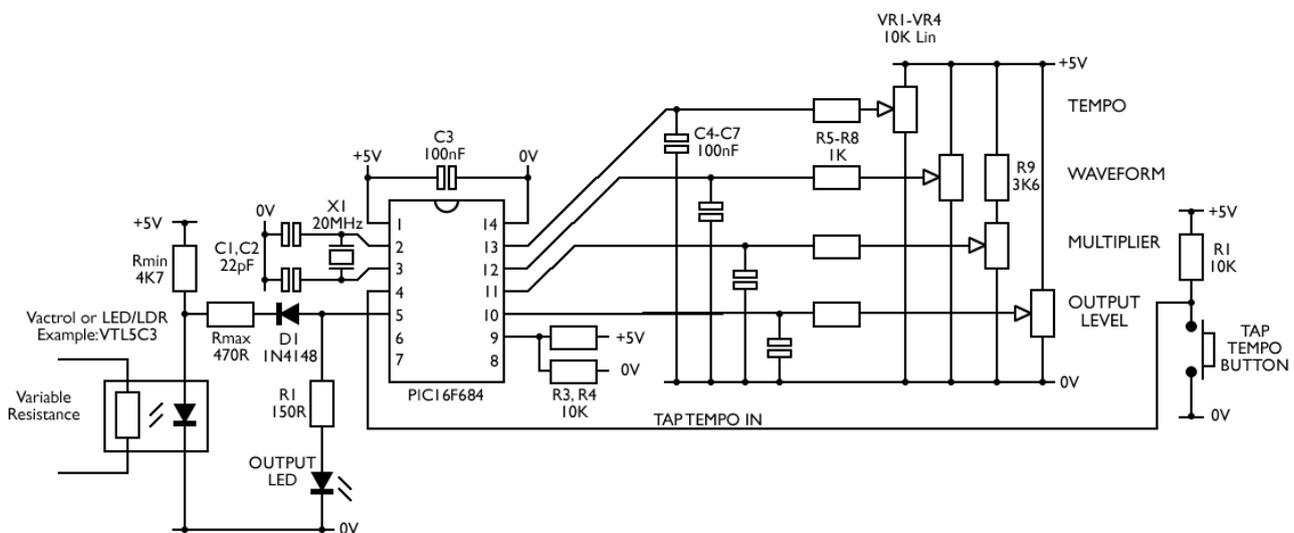
The PWM output from the chip is ideal for controlling the LED in a vactrol. LEDs don't have a linear current/brightness response, which means controlling them with a typical voltage-output LFO via a resistor gives poor results. Controlling the LEDs brightness with PWM provides much better linearity.



Rmin and Rmax control the minimum and maximum brightness of the LED. Rmin sets the current through the LED when the LFO output is at its lowest level. When the LFO output is at its highest level, the voltage on pin 5 is +5V, so Rmin and Rmax are effectively in parallel. The example VTL5C3 vactrol gives a variable resistance from 60K to 3K3 with the values given.

The variable resistance output can be used instead of, or in parallel with, potentiometers to control parameters in a wide range of circuits. For example, across the 'delay time' pot in a PT2399-based delay for LFO-modulated delay effects.

Tap tempo tremolo circuit

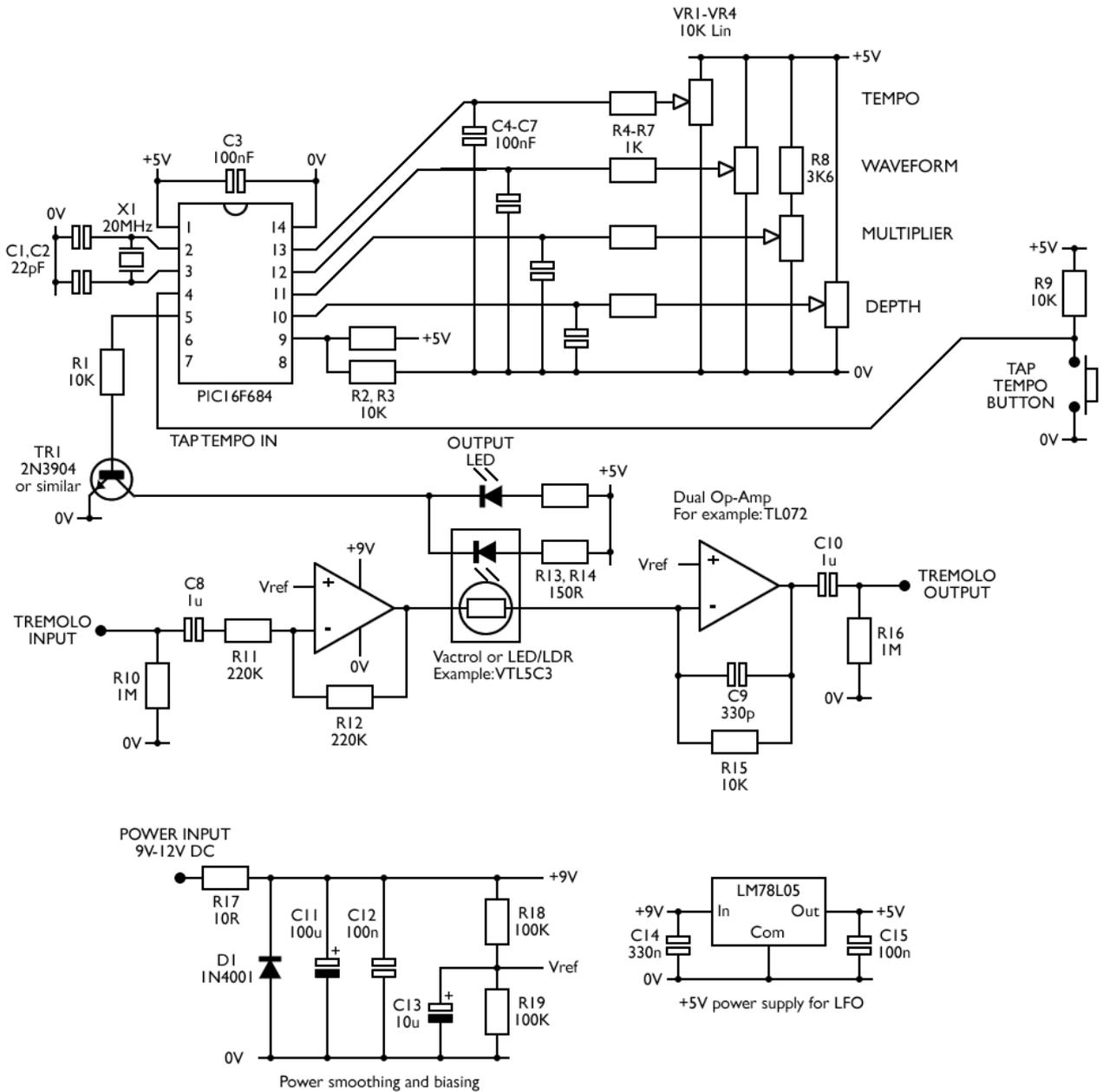

This example circuit shows a complete tremolo effect based on the tap tempo LFO. The tremolo audio path is a clean, simple design based on the classic Tremulus Lune. Thanks to Mike for his work designing this with my original PICVCLFO.

Disabling unwanted CV inputs

If the PULSE WIDTH CV input is not required, it can be tied to a fixed voltage. For a square wave output, this should be 2.5V. This can be produced by a pair of 10K resistors wired as a potential divider between 0V and +5V.


If the LEVEL CV input is not required, it can be disabled by tying the input to the +5V rail with a 10K resistor.

If the MULTIPLIER CV input is not required, it can be tied to a fixed voltage. Since multiplier CVs above 3.75V default to 'x1', the input can be disabled by tying it to the +5V rail with a 10K resistor.

Using rotary switches to select waveform or multiplier

Rotary switches can be used to select waveforms or multipliers by replacing the CV potentiometer with a resistor string that provides the correct voltages, as shown. Since the CV range for each option is fairly wide, exact values are not crucial, but the top and bottom resistors should be roughly half the other value.

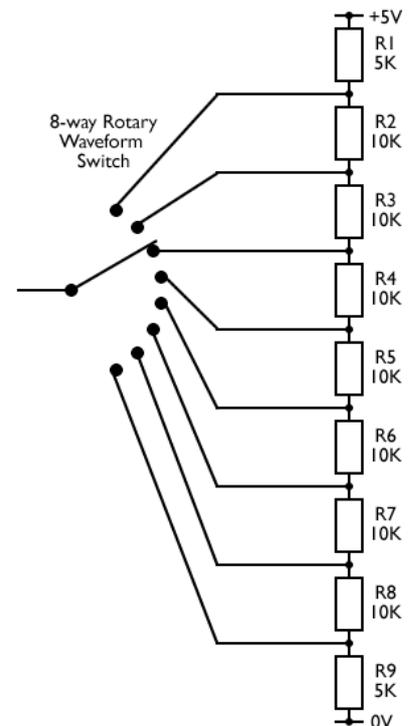The top two options are not used for the Multiplier.



Using the Tap Tempo LFO as a synch-able LFO

The TAP TEMPO input accepts negative-going 5-0V pulses, and times the period between the falling edges of consecutive pairs of pulses to set the frequency. If another device provides a 0-5V clock signal, this can be fed to the TAP TEMPO input and the LFO will synchronize to the clock.

The circuit shown can be used to provide an input that is safe for sync pulses up to about 20V.

